

Experiment 4: Series and Parallel Circuits

PHYS LAB 2240

Simon Xiang

Physics Lab Section 502
University of North Texas
February 21, 2020

1 Abstract

The objective of this experiment was to show the inner workings of circuits in parallel and series and calculate their respective equivalent resistances. To do this, four circuits were set up, giving the experimenter hands on circuit experience in the laboratory. Another objective of this experiment was to show how lightbulbs behaved when connected in series and in parallel.

Our results were extremely precise and reflected the accuracy of the theoretical formula for deriving R_{eq} as opposed to the experimental method. The average percent difference between the two R_{eq} values across all four circuit diagrams was 1.29%, showing that our experimental results are consistent with Ohm's Law due to the extremely low percent difference. This experiment's significance is that it demonstrates one of the most fundamental laws in physics (Ohm's Law), shows how to calculate resistance of circuits in series and parallel, and gives hands on experience in the lab, with future applications including setting up circuits and anything involving resistors.

2 Introduction

Several fundamental concepts are demonstrated within this experiment. The first is Ohm's Law, mathematically given by the formula

$$V = IR, \quad (1)$$

where V is the voltage through a given conductor, I is the current through such conductor, and R being defined as the ratio V/I . The voltage V is measured in volts ($1V = 1\frac{J}{C}$), the current I is measured in amperes ($1A = 1\frac{C}{s}$), and the resistance R is measured in ohms ($1\Omega = 1\frac{V}{A} = 1\frac{J \cdot s}{C^2}$).

In the case of a device that obeys Ohm's Law, such resistance R is constant, and such devices are said to be Ohmic. Resistors are known to be Ohmic. We define an **equivalent resistor** as a resistor that can replace a more complex circuit, i.e., produce the same amount of current when the same amount of voltage is applied. Refer to Figure 1 for the circuit diagram of two resistors in series: We have by the conservation of energy

$$V = V_1 + V_2$$

for two resistors in series. Consider Ohm's Law: since $V_1 = IR_1$, $V_2 = IR_2$, we have

$$V = IR_1 + IR_2 = I(R_1 + R_2).$$

So

$$R_1 + R_2 = \frac{V}{I},$$

and we conclude that

$$R_{eq} = R_1 + R_2. \quad (2)$$

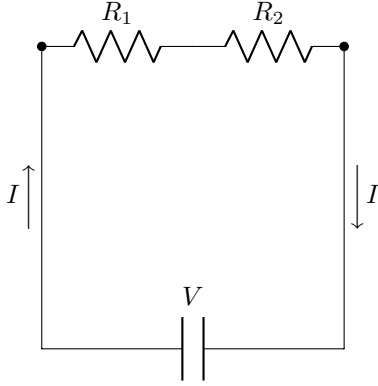


Figure 1: Resistors in series.

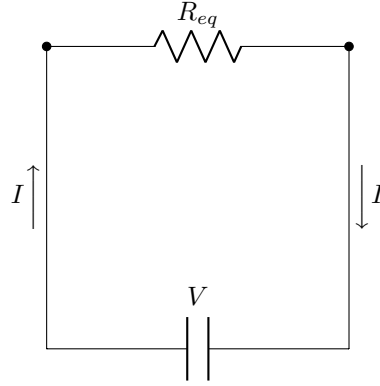


Figure 2: Equivalent resistor.

This can be represented by the following circuit diagram analogous to Figure 1, shown in Figure 2. In the case that the resistors are in parallel, we have

$$V = V_1 = V_2,$$

since each resistor receives all the current. Refer to the circuit diagram given by Figure 3 for more information. By Ohm's Law and the conservation of charge, we have

$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2},$$

therefore

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{I}{V},$$

so we can safely conclude that

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$

Some simple algebra yields the equation

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}. \quad (3)$$

See Figure 4 for an example of what the equivalent resistor for resistors in parallel look like.

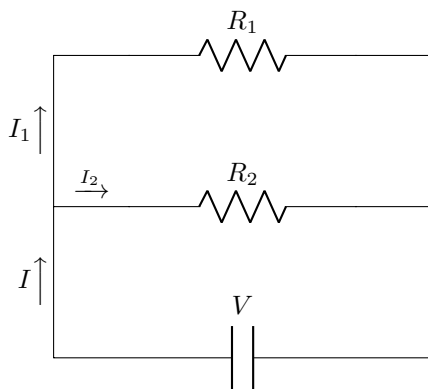


Figure 3: Resistors in parallel.

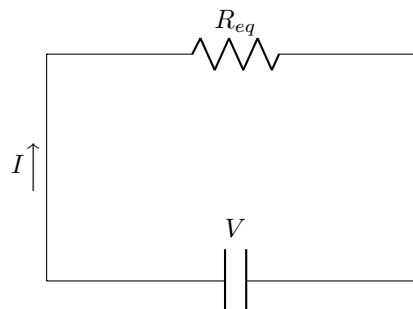


Figure 4: Equivalent resistor for resistors in parallel.

3 Apparatus

Apparatus used include an AC/DC Electronics lab, a Digital Storage Oscilloscope and its probes, a DMM (Digital Multimeter), a DC Power Supply, six resistors, and three lightbulbs.


The six resistor bands came in two sets of three resistance levels, being 330Ω , 560Ω , and 1000Ω respectively. The DMM was crucial in experimentally determining the resistance of such resistors and verifying whether they fell within the percent error indicated by the color of the last band of the resistor ($\pm 5\%$ for this experiment). The DMM also measured the current of the entire circuit, powered by the DC power supply itself. Finally, current was provided to the lightbulbs to demonstrate how they changed (or didn't) in brightness as current varied for the last portion of the experiment.

4 Experimental Procedure

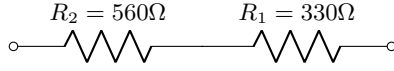
Part A: Series and Parallel Resistor Circuits

Preceding the experiment, the DMM was used to measure the resistance values for the six resistors and verify that they indeed fell within the given percent error indicated by the color of the last band on the resistors.


Consider the following four circuit diagrams on the page below- we will refer to them heavily when describing the experimental procedure.




Circuit Diagram 1: Series

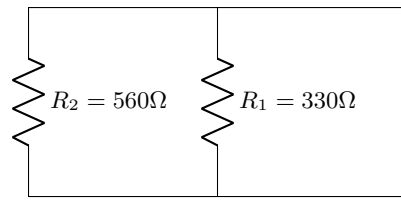

Circuit Diagram 2: Parallel

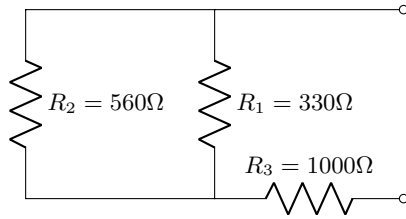

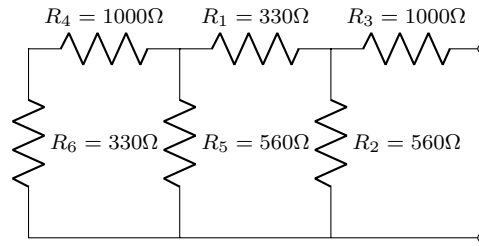Circuit Diagram 3: Simple Series Parallel



Circuit Diagram 4: Complex Series Parallel

The experiment began by setting up the circuit according to Circuit Diagram 1 above. Following, the DMM was inserted **in series**, since the circuit was set up in series. After adjusting the DMM to the proper units (mA), the DC power supply was activated and a quick check was done to see that both the voltage and current were set to zero by turning their respective knobs to zero on the power supply. Then, the power supply and DMM were connected to the circuit, and the voltage on the DC Power Supply was set to $15.00V$. Using the current knob, the current was **slowly** increased with small additions (about $0.010A$) until a voltage of $15.00V$ was reached. From this, the DMM was used to measure the current, and the power supply was turned off.

In terms of calculations, the *theoretical* R_{eq} was calculated by referring to Equation 2 since the circuit was set up in series. Particular care was taken in making sure that the measured values were used for the resistance as opposed to the given base values. The *measured* R_{eq} was calculated by Ohm's law (Equation 1). Then, the percent difference between the two values was calculated using the handy formula

$$\text{Percent Difference} = \frac{|theoretical - measured|}{\frac{|theoretical + measured|}{2}} \cdot 100\%. \quad (4)$$

Now the circuit was disassembled and re-setup in the pattern of Circuit Diagram 2, in parallel. Everything following the step when the voltage on the DC Power Supply was set to $15.00V$ was repeated for the newly setup circuit. Something particular to note was that the theoretical R_{eq} was calculated using Equation 3

as opposed to Equation 2 since the circuit was set up in parallel. This pattern followed for Circuit Diagrams 3 and 4. For Circuit Diagram 3, the theoretical R_{eq} was calculated by first considering R_1 and R_2 in parallel, then considering the resultant R_{eq} in series with R_3 . This is shown in Equation 5 in the Calculations section below. For Circuit Diagram 4, R_4 and R_6 were considered in series, then the resultant equivalent resistor was considered in parallel with R_5 . Then, such resultant equivalent resistor was considered in series with R_1 , which was then considered in parallel with R_2 , which was then finally considered in series with R_3 to complete the calculation of the equivalent resistor of the entire circuit, represented by Equation 6.

A detailed mathematical representation of these calculations can be found in the Calculations section of this report.

Part B: Series and Parallel Lightbulb Circuits

Unfortunately I am unaware of the capabilities of L^AT_EX to generate lightbulb figures, so the terms "series", "parallel", and "series parallel" will have to do when describing the setup of the circuit board. We begin by connecting lightbulb A in series to the power supply and setting the voltage to 2.00V. Once again, we slowly increase the current to reach 2.00V (we expect to end somewhere about 0.260A). Using the values *displayed on the power supply*, we determine the resistance of A by Ohm's Law (Equation 1). Rinse and repeat for lightbulbs B and C. After determining the resistance of all three bulbs, set up the lightbulbs A and B in series and determine the resistance. Then, set up lightbulbs A and B in parallel and determine the resistance. Finally, set up all three lightbulbs in the series parallel setup and determine the resistance.

Some issues included a resistor breaking in half halfway through the experiment, and the peculiar case of the lightbulbs lighting up in the wrong order even with a correct setup as verified by our lab TA's. The first problem was resolved by grabbing a new resistor from another table since we hadn't used that particular resistor yet at that point in time. The second problem was never resolved.

5 Data

Table 1: Data obtained from measuring the resistance values of the six given resistors with the DMM. These values were used to calculate the theoretical resistance in junction with the derived equations for R_{eq} .

$R_1 = 330\Omega$	$R_2 = 560\Omega$	$R_3 = 1000\Omega$	$R_4 = 1000\Omega$	$R_5 = 560\Omega$	$R_6 = 330\Omega$
325.5 Ω	544 Ω	978 Ω	980 Ω	552 Ω	324.3 Ω

Table 2: Data obtained from experimentally determining the value(s) of R_{eq} for each circuit diagram. Here, the data from Table 1 was used to calculate the theoretical R_{eq} , the measured current and R_{eq} were experimentally determined in junction with Ohm's Law (with V being a constant $15V$, see Equation 1), and the percent difference was calculated with Equation 4. These calculations are all shown in the manual calculation section of this lab report.


Circuit Diagram	Theoretical $R_{eq}(\Omega)$	Measured Current (mA)	Measured $R_{eq}(\Omega)$	Percent Difference
1	869.5	17.1	877.2	0.88%
2	203.65	71.2	210.7	3.39%
3	1181.65	12.6	1190.5	0.74%
4	1291.28	11.6	1293.1	0.14%

Table 3: Finally we reach the table of data for the lightbulb portion of this experiment. These values are entirely experimental and were all measured from the reading off of the power supply and letting the voltage V equal two volts and solving for resistance by Ohm's Law.

Bulb System	Measured Resistance (Ω)
A	7.38
B	8.13
C	15.873
A&B Series	10.582
A&B Parallel	3.914
Series Parallel	8.811

6 Calculations

We begin this section by deriving the precise mathematical formulas for the calculation of the respective R_{eq} 's for each circuit diagram. Consider Circuit Diagram 1 and 2. Clearly the resistors are simply in series or parallel, so a direct application of Equation 2 and 3 will suffice in calculating the R_{eq} for these circuit diagrams. Let us turn our attention to Circuit Diagram 3, once again displayed for clarity:

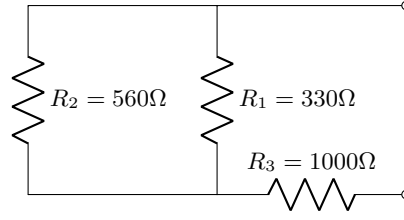

Circuit Diagram 3: Simple Series Parallel


Now clearly the resistors R_1 and R_2 are in parallel, so we apply Equation 3 to obtain

$$R_{eq(1)} = \frac{R_1 R_2}{R_1 + R_2}.$$

From here, the resultant equivalent resistor is in series with the resistor R_3 , so we apply Equation 2 to obtain

$$R_{eq} = R_{eq(1)} + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3 \quad (5)$$

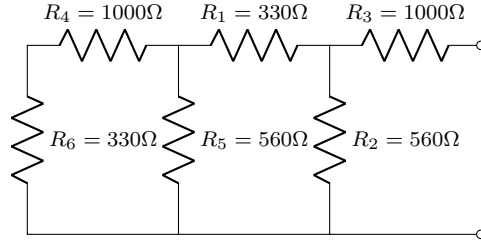to obtain the R_{eq} for the entirety of the system in Circuit Diagram 3. Now let us turn our attention once more to Circuit Diagram 4 below:



Circuit Diagram 4: Complex Series Parallel

This indeed is a very complex setup. The resulting formula will be quite nasty, but do not fear, as solving for R_{eq} iteratively by plugging in values obtained at each step is much simpler. However, we will still write an expression for the formula in terms of the given quantities for the sake of mathematical purity. We have resistors R_4 and R_6 in series, so

$$R_{eq(1)} = R_4 + R_6.$$

Then we take $R_{eq(1)}$ in parallel with R_5 and we get

$$R_{eq(2)} = \frac{R_{eq(1)} R_5}{R_{eq(1)} + R_5} = \frac{(R_4 + R_6) R_5}{R_4 + R_5 + R_6}.$$

We repeat, taking $R_{eq(2)}$ in series with R_1 , yielding

$$R_{eq(3)} = R_{eq(2)} + R_1 = \frac{(R_4 + R_6)R_5}{R_4 + R_5 + R_6} + R_1,$$

and so the resultant equivalent resistor is in parallel with R_2 , so yet another application of Equation 3 yields

$$R_{eq(4)} = \frac{R_{eq(3)} R_2}{R_{eq(3)} + R_2} = \frac{\left(\frac{(R_4 + R_6)R_5}{R_4 + R_5 + R_6} + R_1\right) R_2}{\frac{(R_4 + R_6)R_5}{R_4 + R_5 + R_6} + R_1 + R_2}.$$

Finally, we take $R_{eq(4)}$ in series with R_3 to obtain the final expression

$$R_{eq} = R_{eq(4)} + R_3 = \frac{\left(\frac{(R_4 + R_6)R_5}{R_4 + R_5 + R_6} + R_1\right) R_2}{\frac{(R_4 + R_6)R_5}{R_4 + R_5 + R_6} + R_1 + R_2} + R_3. \quad (6)$$

Our fruitless toil comes to a conclusion.

Manual Calculations

Now we begin the menial task of plugging in numbers into these formulas to get theoretical values for R_{eq} . We use the data from Table 1, which we once again show for clarity:

$R_1 = 330\Omega$	$R_2 = 560\Omega$	$R_3 = 1000\Omega$	$R_4 = 1000\Omega$	$R_5 = 560\Omega$	$R_6 = 330\Omega$
325.5 Ω	544 Ω	978 Ω	980 Ω	552 Ω	324.3 Ω

Now calculating R_{eq} for Circuit Diagrams 1 and 2 is trivial: take Equations 2 and 3 respectively and simply plug in the data from the table. For Circuit Diagram 1, we have

$$R_{eq} = 325.5 + 544 = 869.5,$$

and for Circuit Diagram 2 we have

$$R_{eq} = \frac{325.5 \cdot 544}{325.5 + 544} = 203.65.$$

Plug in the values of Table 1 into Equation 5 to obtain

$$R_{eq} = \frac{325.5 \cdot 544}{325.5 + 544} + 978 = 1181.65$$

for Circuit Diagram 3. For Circuit Diagram 4, we use the obtrusively long Equation 6 to get

$$R_{eq} = \frac{\frac{(980+324.3)552}{980+552+324.3} + 325.5}{\frac{(980+324.3)552}{980+552+324.3} + 325.5 + 544} + 978 = 1291.28.$$

Now that we have finished calculating the theoretical R_{eq} 's, we turn our attention to manually calculating the measured R_{eq} 's by Ohm's Law. Ohm's Law (or Equation 1) states that $V = IR$, or $R = \frac{V}{I}$. Here the voltage remains at a constant $15V$, so for Circuit Diagram 1, $R_{eq} = \frac{15V}{17.1mA} = 877.2\Omega$, $R_{eq} = \frac{15V}{71.2mA} = 210.7\Omega$ for Circuit Diagram 2, $R_{eq} = \frac{15V}{12.6mA} = 1190.48\Omega$ for Circuit Diagram 3, and finally $R_{eq} = \frac{15V}{11.6mA} = 1293.1\Omega$ for Circuit Diagram 4.

Calculating percent differences is also a tedious task: apply Equation 4 four times to the data above. For Circuit Diagram 1, we have

$$\text{Percent Difference} = \frac{|869.5 - 877.2|}{\frac{|869.5 + 877.2|}{2}} \cdot 100\% = 0.88\%,$$

for Circuit Diagram 2

$$\text{Percent Difference} = \frac{|203.65 - 210.7|}{\frac{|203.65 + 210.7|}{2}} \cdot 100\% = 3.39\%,$$

for Circuit Diagram 3

$$\text{Percent Difference} = \frac{|1181.65 - 1190.48|}{\frac{|1181.65 + 1190.48|}{2}} \cdot 100\% = 0.74\%,$$

and finally for Circuit Diagram 4

$$\text{Percent Difference} = \frac{|1291.28 - 1293.1|}{\frac{|1291.28 + 1293.1|}{2}} \cdot 100\% = 0.14\%,$$

which concludes the calculations portion of this lab report.

7 Discussion of Results and Error Analysis

There are several possible sources of error of this experiment. The first is the inherent internal resistance of the wires and resistors themselves- although theoretically they match up with the Ohm reading indicated in the manual, there will always be a tolerance error of about ($\pm 5\%$) in the resistors themselves. This is indicated by the color of the last band of the resistor, since in this experiment they were all gold, the error was within the ($\pm 5\%$) threshold. Now to further minimize error we used the measured values of the resistance of the resistors to calculate the theoretical R_{eq} 's, however, further sources of error within the experiment persist. One of them is the equipment- things like how accurate the DMM is in measuring current, how close the voltage the power supply puts out is to $15V$, the quality of the circuit board, how strong the lightbulbs are, and so on. In our particular experiment, a faulty circuit board led to confusion in Part B of the experiment- the lightbulb not receiving the current first shone much brighter than the one that was supposed to be brighter.

Furthermore, the ambient temperature of the room also affects current and therefore voltage and resistance. Conditions will never be 100% ideal, and

therefore there will always be error within the experiment. However, our results were relatively good, with extremely low percent differences, the lowest being 0.14% and the highest being 3.39%, which is still incredibly low (and much much higher than the other percent differences too). The average percent difference was 1.29%, showing that even with the many sources of error listed above the experiment prove to be quite accurate and true to the theoretical results.

8 Conclusion

It appears as if it is time for this lab report to reach a conclusion. We have considered several equations of relative importance, such as Ohm's Law and resistors in series and parallel, and learned about equivalent resistors and how they can be used to simply resistor circuit calculations. We verified that the resistance of resistors in series added additively, while resistors in parallel added reciprocally experimentally. We also studied more complex circuit diagrams and dove into how to calculate equivalent resistors for such systems. There was also a section demonstrating the effect of current on the strength of various lightbulbs.

Based off of the extremely low percent errors, our results seem to completely support the theory behind the calculation of R_{eq} for various resistor setups. Such errors can possibly be eliminated or reduced with better equipment, ideal room conditions, and more precise resistors. However not all of these options are available to an undergraduate physics lab section (some may not even be available to research labs), and yet our measured results were still quite spot on with the theoretical values calculated. This means that the method used is precise enough to obtain such a low percent error (average of 1.29%), and therefore sufficiently accurate. We conclude that resistors do indeed follow Ohm's Law, equivalent resistors for resistors in series and parallel are indeed calculated the way that we derived in the introduction, and that modern physics as we know it is indeed somewhat accurate.